

High pass filter

R1 OUT 0 10k

C1 in OUT 470n

Vin in 0 DC 5 sin(0 5 1k 0 0)

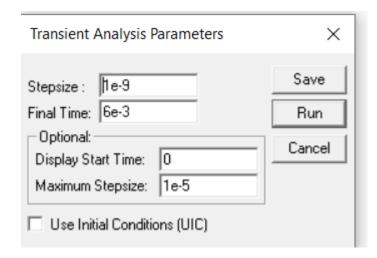

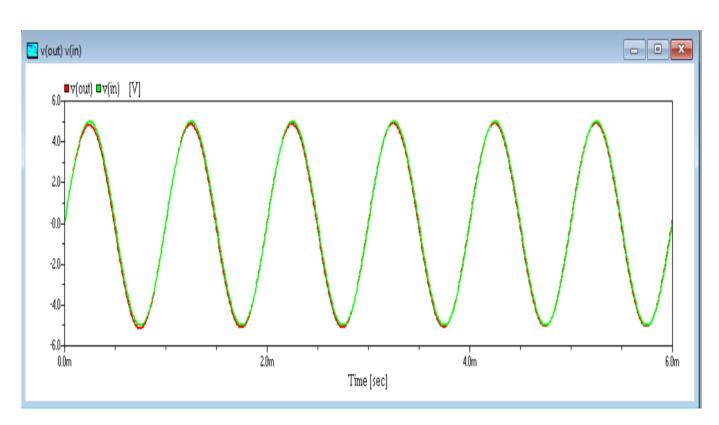

High pass filter


HPF - high pass filter


R1 OUT 0 10k

C1 in OUT 470n

!Vin in 0 DC 5 sin(0 5 1k 0 0)

Vin in 0 DC 5 sin(0 5 12 0 0)

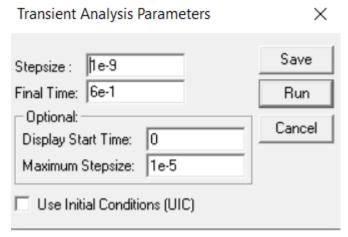

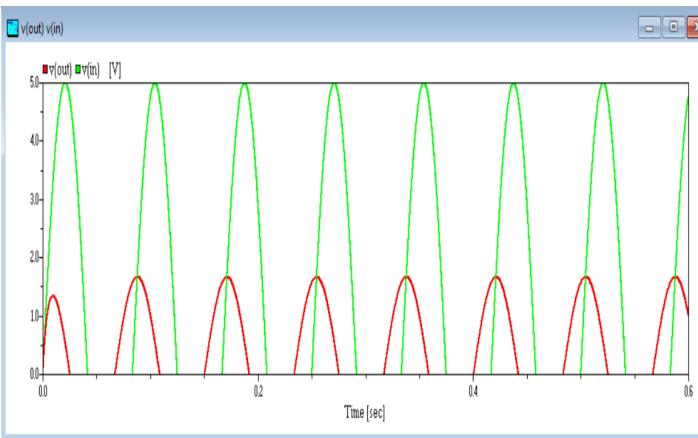


Low pass filter


LPF - low pass filter

C1 OUT 0 470n

R1 in OUT 10k

Vin in 0 DC 5 sin(0 5 1k 0 0)

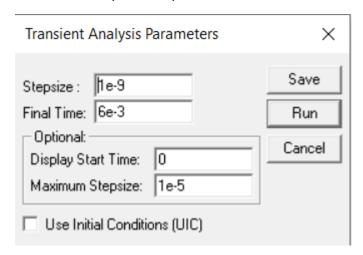

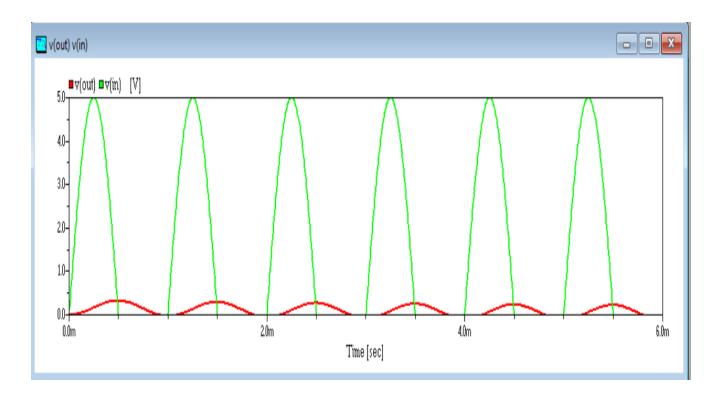

Low pass filter

LPF - low pass filter

C1 OUT 0 470n

R1 in OUT 10k

!Vin in 0 DC 5 sin(0 5 1k 0 0)

Vin in 0 DC 5 sin(0 5 12 0 0)

